

## PREVIEW QUESTION BANK

Module Name : nou24-ec03 Digital electronic and System design-ENG  
Exam Date : 18-May-2024 Batch : 15:00-18:00

Sr. No.	Client Question ID	Question Body and Alternatives	Marks	Negative Marks
Objective Question				
1	13202001	<p>The <math>(100110)_2</math> is numerically equivalent to</p> <ol style="list-style-type: none"> <li>1. <math>(26)_{16}</math></li> <li>2. <math>(36)_{10}</math></li> <li>3. <math>(46)_8</math></li> <li>4. <math>(212)_4</math></li> </ol> <p>The correct answer are</p> <ol style="list-style-type: none"> <li>1. 1, 2, and 3</li> <li>2. 2, 3, and 4</li> <li>3. 1, 2, and 4</li> <li>4. 1, 3, and 4</li> </ol> <p>A1 : 1</p> <p>A2 : 2</p> <p>A3 : 3</p> <p>A4 : 4</p>	2.0	0.00
Objective Question				
2	13202002	<p>If <math>(211)_x = (152)_8</math>, then the value of base x is</p> <ol style="list-style-type: none"> <li>1. 6</li> <li>2. 5</li> <li>3. 7</li> <li>4. 9</li> </ol> <p>A1 : 1</p> <p>A2 : 2</p> <p>A3 : 3</p> <p>A4 : 4</p>	2.0	0.00
Objective Question				
3	13202003		2.0	0.00

Which gates in Digital Circuits are required to convert a NOR-based SR latch to an SR flip-flop?

1. Two 2 input AND gates
2. Two 3 input AND gates
3. Two 2 input OR gates
4. Two 3 input OR gates

A1 : 1

A2 : 2

A3 : 3

A4 : 4

Objective Question

4 13202004

When does a negative level triggered flip-flop in Digital Electronics changes its state?

1. When the clock is negative
2. When the clock is positive
3. When the inputs are all zero
4. When the inputs are all one

A1 : 1

A2 : 2

A3 : 3

A4 : 4

2.0 0.00

Objective Question

5 13202005

What is the binary subtraction of  $101001 - 010110 = ?$

1. 010011
2. 100110
3. 011001
4. 010010

A1 : 1

A2 : 2

A3 : 3

A4 : 4

2.0 0.00

Objective Question

6 13202006

2.0 0.00

The simplified form of a logic function  $Y = A(B + C(\overline{AB} + AC))$  is

- 1. A'B'
- 2. AB
- 3. A'B
- 4. AB'

A1 : 1

A2 : 2

A3 : 3

A4 : 4

Objective Question

7 13202007

The inputs of a NAND gate are connected together. The resulting circuit is .....

- 1. OR
- 2. NOT
- 3. AND
- 4. NAND

A1 : 1

A2 : 2

A3 : 3

A4 : 4

2.0 0.00

Objective Question

8 13202008

In 2's complement representation the number 11100101 represents the decimal number .....

- 1. +37
- 2. -31
- 3. +27
- 4. -27

A1 : 1

A2 : 2

A3 : 3

A4 : 4


2.0 0.00

Objective Question

9 13202009

 2.0 0.00

For the gate in the given figure the output will be .....



1. 0
2. 1
3. A
4. A'

A1 : 1

A2 : 2


A3 : 3

A4 : 4

Objective Question

10 13202010

 The circuit of the given figure realizes the function .....



1.  $Y = (\bar{A} + \bar{B}) C + \bar{D}E$
2.  $Y = \bar{A} + \bar{B} + \bar{C} + \bar{D} + \bar{E}$
3.  $AB + C + DE$
4.  $AB + C(D + E)$

A1 : 1

A2 : 2

A3 : 3

A4 : 4

Objective Question

11 13202011

An AND gate has two inputs A and B and one inhibit input S, Output is 1 if

1. A = 1, B = 1, S = 1
2. A = 1, B = 1, S = 0
3. A = 1, B = 0, S = 1
4. A = 1, B = 0, S = 0

A1 : 1

A2 : 2

A3 : 3

A4 : 4

## Objective Question

12 13202012

Which of the following is NOT a type of component available in Tinkercad Circuits?

1. Resistors
2. Transistors
3. Motors
4. Capacitors

A1 : 1

A2 : 2

A3 : 3

A4 : 4

2.0 0.00

## Objective Question

13 13202013

What is the purpose of the "Start Simulation" button in Tinkercad Circuits?

1. To export the circuit diagram
2. To print a 3D model of the circuit
3. To run a real-time simulation of the circuit behavior
4. To save the circuit to the user's profile

A1 : 1

A2 : 2

A3 : 3

A4 : 4

2.0 0.00

## Objective Question

14 13202014

Which tool in Tinkercad Circuits allows users to measure voltage and current at different points in the circuit?

1. Multimeter
2. Oscilloscope
3. Function generator
4. Battery

A1 : 1

A2 : 2

2.0 0.00

A3 : 3

A4 : 4

Objective Question

15 13202015

For the minterm designation  $Y = \sum m(1, 3, 5, 7)$  the complete expression is .....

2.0 0.00

1.  $Y = \bar{A} \bar{B} C + A \bar{B} C$
2.  $Y = \bar{A} \bar{B} C + A \bar{B} C + ABC + \bar{A} BC$
3.  $Y = \bar{A} \bar{B} \bar{C} + \bar{A} \bar{B} C + \bar{A} BC + A \bar{B} C$
4.  $Y = \bar{A} \bar{B} \bar{C} + ABC + \bar{A} \bar{B} C + A \bar{B} C$

A1 : 1

A2 : 2

A3 : 3

A4 : 4

Objective Question

16 13202016

For the K map in the given figure the simplified Boolean expression is .....

2.0 0.00

	CD	00	01	11	10
AB	00				
01			1		
11			1	1	
10				1	

1.  $\bar{A} \bar{C} + \bar{A} \bar{D} + ABC$
2.  $\bar{A} C + \bar{A} \bar{D} + ABC$
3.  $\bar{A} C + \bar{A} \bar{D} + ACD$
4.  $\bar{A} \bar{C} + \bar{A} \bar{D} + AB \bar{C}$

A1 : 1

A2 : 2

A3 : 3

A4 : 4

Objective Question

17 13202017

2.0 0.00

In a BCD to 7 segment decoder the minimum and maximum number of outputs active at any time is ....

1. 2 and 7
2. 3 and 7
3. 1 and 6
4. 3 and 6

A1 : 1

A2 : 2

A3 : 3

A4 : 4

Objective Question

18 13202018

2.0 0.00

Which of the following logic families typically offers the highest speed performance?

1. TTL
2. ECL
3. CMOS
4. NMOS

A1 : 1

A2 : 2

A3 : 3

A4 : 4

Objective Question

19 13202019

2.0 0.00

Which of the following is a characteristic of CMOS logic gates?

1. High input impedance
2. High output impedance
3. Low noise immunity
4. High power consumption

A1 : 1

A2 : 2

A3 : 3

A4 : 4

Objective Question

20 13202020

2.0 0.00

Which component of the ALU is responsible for selecting the specific operation to be performed?

1. Multiplexer
2. Comparator
3. Decoder
4. Control Unit

A1 : 1

A2 : 2

A3 : 3

A4 : 4

Objective Question

21 13202021

What is the primary function of a multiplexer (MUX) in a combinational circuit?

1. Adding numbers
2. Selecting one of many inputs based on control signals
3. Performing logical AND operation
4. Storing data temporarily

A1 : 1

A2 : 2

A3 : 3

A4 : 4

2.0 0.00

Objective Question

22 13202022

Which type of ADC is known for its high accuracy but slower conversion speed?

1. Flash ADC
2. Successive approximation ADC
3. Delta-sigma ADC
4. Dual-slope integration ADC

A1 : 1

A2 : 2

A3 : 3

A4 : 4

2.0 0.00

Objective Question

23 13202023

2.0 0.00



Which logic family is known for its low power consumption but suffers from poor noise immunity?

1. TTL
2. CMOS
3. ECL
4. NMOS

A1 : 1

A2 : 2

A3 : 3

A4 : 4

Objective Question

24 13202024

Which of the following gate is represented by the Boolean expression  $F = (A'+B)'$

1. OR GATE
2. EX-OR GATE
3. AND GATE
4. NOT GATE

A1 : 1

A2 : 2

A3 : 3

A4 : 4

2.0 0.00

Objective Question

25 13202025

The dual of  $A.A' = 0$  is

1.  $A+A' = 1$
2.  $A'.A = 1$
3.  $A+A' = 0$
4.  $A'+A = 0$

A1 : 1

A2 : 2

A3 : 3

A4 : 4

2.0 0.00

Objective Question

26 13202026

2.0 0.00

In which logic family does the output voltage directly switch between the power supply rails?

1. TTL
2. CMOS
3. ECL
4. NMOS

A1 : 1

A2 : 2

A3 : 3

A4 : 4

Objective Question

27 13202027

Which binary code is also known as the weighted code?

1. Excess-3 code
2. Gray code
3. BCD Code
4. ASCII Code

A1 : 1

A2 : 2

A3 : 3

A4 : 4

2.0 0.00

Objective Question

28 13202028

In digital logic, a counter is a device which \_\_\_\_\_

1. Counts the number of outputs
2. Stores the number of times a particular event or process has occurred
3. Stores the number of times a clock pulse rises and falls
4. Counts the number of inputs

A1 : 1

A2 : 2

A3 : 3

A4 : 4

2.0 0.00

Objective Question

29 13202029

2.0 0.00

What is the maximum possible range of bit-count specifically in n-bit binary counter consisting of 'n' number of flip-flops?

1. 0 to  $2^n$
2. 0 to  $2^n + 1$
3. 0 to  $2^n - 1$
4. 0 to  $2^{n+1/2}$

A1 : 1

A2 : 2

A3 : 3

A4 : 4

Objective Question

30 13202030 2.0 0.00

Ripple counters are also called \_\_\_\_\_

1. SSI counters
2. Asynchronous counters
3. Synchronous counters
4. VLSI counters

A1 : 1

A2 : 2

A3 : 3

A4 : 4

Objective Question

31 13202031 2.0 0.00

Three decade counter would have \_\_\_\_\_

1. 2 BCD counters
2. 3 BCD counters
3. 4 BCD counters
4. 5 BCD counters

A1 : 1

A2 : 2

A3 : 3

A4 : 4

Objective Question

32 13202032 2.0 0.00

The full form of SIPO is \_\_\_\_\_

1. Serial-in Parallel-out
2. Serial-in Process-out
3. Serial-in Perepheral-out
4. Serial-in Public-out

A1 : 1

A2 : 2

A3 : 3

A4 : 4

Objective Question

33 13202033 2.0 0.00

A shift register that will accept a parallel input or a bidirectional serial load and internal shift features is called as?

1. Tristate
2. End around
3. Universal
4. Conversion

A1 : 1

A2 : 2

A3 : 3

A4 : 4

Objective Question

34 13202034 2.0 0.00

How can parallel data be taken out of a shift register simultaneously?

1. Use the Q output of the first FF
2. Use the Q output of the last FF
3. Tie all of the Q outputs together
4. Use the Q output of each FF

A1 : 1

A2 : 2

A3 : 3

A4 : 4

Objective Question

35 13202035 2.0 0.00

The group of bits 11001 is serially shifted (right-most bit first) into a 5-bit parallel output shift register with an initial state 01110. After three clock pulses, the register contains

1. 01110
2. 00001
3. 00101
4. 00110

A1 : 1

A2 : 2

A3 : 3

A4 : 4

Objective Question

36 13202036

A serial in/parallel out, 4-bit shift register initially contains all 1s. The data nibble 0111 is waiting to enter. After four clock pulses, the register contains

1. 0000
2. 1111
3. 0111
4. 1000

A1 : 1

A2 : 2

A3 : 3

A4 : 4

2.0 0.00

Objective Question

37 13202037

Which of the following method is employed for ADC?

1. Ladder network
2. Successive approximation type
3. PWM type
4. None of the mentioned

A1 : 1

A2 : 2

A3 : 3

A4 : 4

2.0 0.00

Objective Question

38 13202038

2.0 0.00

Latches constructed with NOR and NAND gates tend to remain in the latched condition due to which configuration feature?

1. Cross coupling
2. Gate impedance
3. Synchronous operation
4. Low input voltages

A1 : 1

A2 : 2

A3 : 3

A4 : 4

Objective Question

39 13202039 2.0 0.00

The truth table for an S-R flip-flop has how many VALID entries?

1. 1
2. 2
3. 3
4. 4

A1 : 1

A2 : 2

A3 : 3

A4 : 4

Objective Question

40 13202040 2.0 0.00

Which circuit is generated from D flip-flop due to addition of an inverter by causing reduction in the number of inputs?

1. Gated JK-latch
2. Gated D-latch
3. Gated T-latch
4. Gated SR-latch

A1 : 1

A2 : 2

A3 : 3

A4 : 4

Objective Question

41 13202041 2.0 0.00

Two J-K flip-flops with their J-K inputs tied HIGH are cascaded to be used as counters. After four input clock pulses, the binary count is

1. 00
2. 11
3. 01
4. 10

A1 : 1

A2 : 2

A3 : 3

A4 : 4

Objective Question

42 13202042

Which statement describes the BEST operation of a negative-edge-triggered D flip-flop?

1. The Q output is ALWAYS identical to the CLK input if the D input is HIGH
2. The logic level at the D input is transferred to Q on NGT of CLK
3. The Q output is ALWAYS identical to the D input when CLK = PGT
4. The Q output is ALWAYS identical to the D input

A1 : 1

A2 : 2

A3 : 3

A4 : 4

2.0 0.00

Objective Question

43 13202043

The only difference between a combinational circuit and a flip-flop is that

1. The flip-flop requires previous state
2. The flip-flop requires next state
3. The flip-flop requires a clock pulse
4. The flip-flop depends on the past as well as present states

A1 : 1

A2 : 2

A3 : 3

A4 : 4

2.0 0.00

Objective Question

44 13202044

2.0 0.00

In JK flip flop same input, i.e. at a particular time or during a clock pulse, the output will oscillate back and forth between 0 and 1. At the end of the clock pulse the value of output Q is uncertain. The situation is referred to as?

1. Conversion condition
2. Race around condition
3. Lock out state
4. Forbidden State

A1 : 1

A2 : 2


A3 : 3

A4 : 4

Objective Question

45 13202045

 Which of the following logic expressions represents the logic diagram shown?



1.  $X=AB'+A'B$
2.  $X=(AB)'+AB$
3.  $X=(AB)'+A'B'$
4.  $X=A'B'+AB$

A1 : 1

A2 : 2


A3 : 3

A4 : 4

Objective Question

46 13202046

The device shown here is most likely a

 

1. Comparator
2. Multiplexer
3. Inverter
4. Demultiplexer



A1 : 1

A2 : 2


A3 : 3

A4 : 4
 
## Objective Question

47 13202047

What type of logic circuit is represented by the figure shown below



1. XOR
2. XNOR
3. AND
4. NAND

A1 : 1

A2 : 2

A3 : 3

A4 : 4

## Objective Question

48 13202048

How many NOT gates are required for the construction of a 4-to-1 multiplexer?

1. 3
2. 4
3. 2
4. 5

A1 : 1

A2 : 2

A3 : 3

A4 : 4

## Objective Question

49 13202049

In 1-to-4 demultiplexer, how many select lines are required

1. 2
2. 3
3. 4
4. 5

A1 : 1

A2 : 2

A3 : 3

A4 : 4

Objective Question

50 13202050

S-R type flip-flop can be converted into D type flip-flop if S is connected to R through

1. OR Gate
2. AND Gate
3. Inverter
4. Full Adder

A1 : 1

A2 : 2

A3 : 3

A4 : 4

2.0 0.00